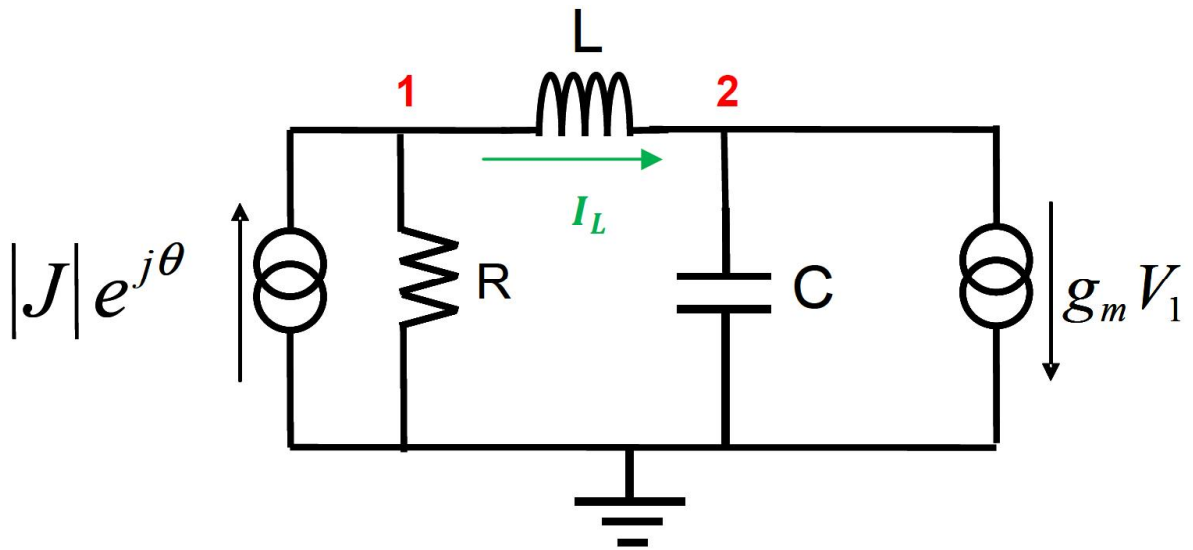


Electrical Circuits, Project #2  
Dr. Sadr, University of Tehran

Question #1:


Write the frequency and time-domain MNA equations for the following circuit.



**Electrical Circuits, Project #2**  
**Dr. Sadr, University of Tehran**

**Question #2:**

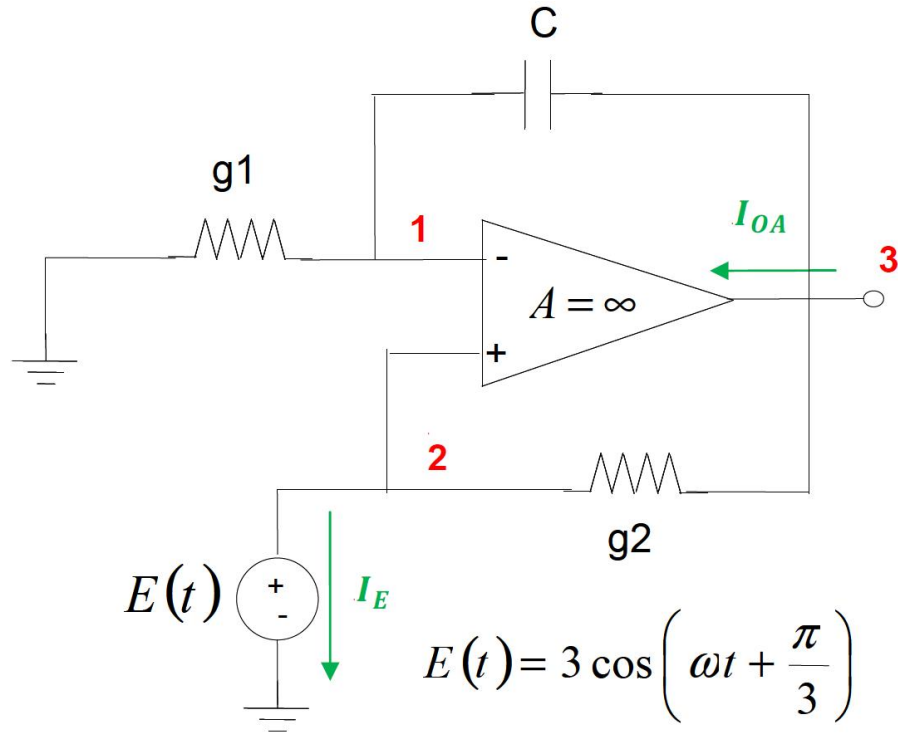**Write the frequency MNA equations for the following circuit.**



If the gain of the operational amplifier as a function of frequency is given by:  $A = \frac{k_1}{s+k_2}$  where  $k_1$  and  $k_2$  are constants, write the time-domain MNA equations for the circuit

**Electrical Circuits, Project #2**  
**Dr. Sadr, University of Tehran**

**Question #3**

**Write a computer program to formulate the frequency domain MNA SPARSE equations in the form  $(G+sC)X = b$**

**Specifications:**

*INPUT:* Netlist in a SPICE-like format or equivalent

*Components:* resistors, capacitors, inductors, voltage sources, current sources, current-controlled voltage sources, voltage-controlled current sources

*OUTPUT:* Frequency response (magnitude and phase)

**Verify manually the correctness of your formulation using simple circuits. Include these circuits in your report.**

#### Question #4

Use the program in (3) and the sparse commands in MATLAB to write a program to compute the frequency response of the circuits shown in Figure 1-2 using LU decomposition and forward/backward substitution.

Plot the response vs frequency. Verify your results using HSPICE (or equivalent).

Plot the sparsity pattern of the MNA matrix before and after the LU decomposition.

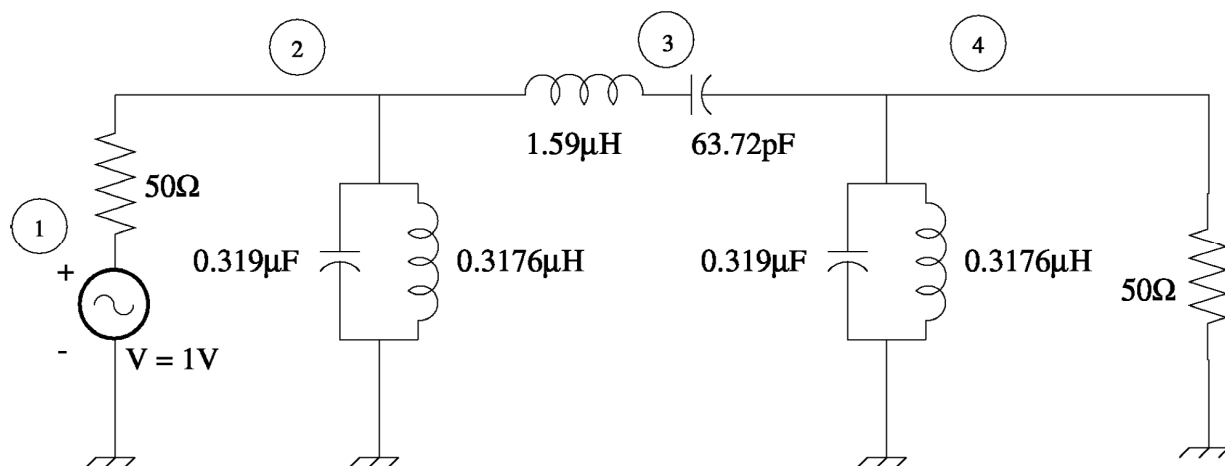


Figure 1.

$R_{1a} = 9,606\Omega$	$C_3 = C_4 = 15\text{nF}$	$V_i = 1V$
$R_{1b} = 23,280\Omega$	$R_3 = R_4 = 9,304\Omega$	
$R_2 = 6.8K\Omega$	$R_q = 52,107\Omega$	Gain of all OpAmps = 50,000
$C_1 = 94.9\text{nF}$	$R_g = 9,304\Omega$	
$C_2 = 20.5\text{nF}$	$r = 20K\Omega$	

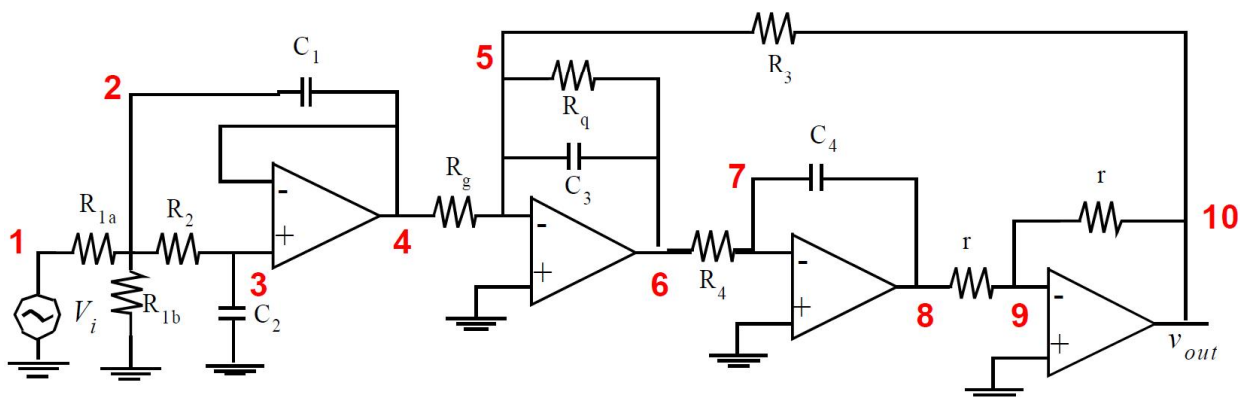


Figure 2.

**Electrical Circuits, Project #2**  
**Dr. Sadr, University of Tehran**

**Question #5**

Consider the linear algebraic equation  $Ax=b$ ; where  $A$  and  $b$  are generated using the listed code. Compare the two following scenarios for solving for  $x$  in terms of memory and CPU time.

**Scenario#1: treat  $A$  as a sparse matrix**

- a) Plot the sparsity pattern of  $A$
- b) Plot the sparsity pattern of the LU factors of  $A$
- c) Find  $x$  and verify its accuracy
- d) Find the CPU time required for the LU decomposition and the F/B substitution.
- e) Plot the CPU time vs.  $n$  for  $1000 < n < 30,000$

**Program:**

```
clear
global A n b
n=4000; %number of nodes
A=sparse(n,n);
b=sparse(n,1);
b(1)=1;
for i=1:n
    if i<=n-5
        A([i,n-4-i],[i,n-4-i])=A([i,n-4-i],[i,n-4-i])+[1,-1;-1,1];
    end
    if i>=6
        A([i,n+5-i],[i,n+5-i])=A([i,n+5-i],[i,n+5-i])+[1,-1;-1,1];
    end
    if i<=n-5
        A([i,i+5],[i,i+5])=A([i,i+5],[i,i+5])+[1,-1;-1,1];
    end
    if i<=n/2
        A([i,n+1-i],[i,n+1-i])=A([i,n+1-i],[i,n+1-i])+[1,-1;-1,1];
    end
end
tic
[L,U,P,Q]=lu(A,0.1);
z=L\(P*b);
Y=U\z;
X=Q*Y;
t=toc;
spy(A)
title('Sparsity of A');
spy(L)
title('Sparsity of L');
spy(U)
title('Sparsity of U');
```